

5-Transistor CMOS Operational Transconductance Amplifier (OTA)

Neeraj Rajesh Piralkar

COEP Technological University, Pune (Formerly College of Engineering Pune)

neeraj102p@gmail.com

eSim Marathon, FOSSEE IIT Bombay


Objective: To design and simulate a 5-transistor CMOS OTA using eSim – 2.5 and analyse its DC operating points, and determine its frequency response and gain characteristics.

Overview: This project details the design, analysis, and optimization of a 5-Transistor (5T) CMOS Operational Transconductance Amplifier (OTA). The design process began with DC analysis to establish the Quiescent Operating Point (Q-point), ensuring all transistors were correctly biased in the saturation region. This initial step included temporary biasing for the output transistor, M5. The final component sizing, including all W/L ratios, was determined during this phase to meet target current specifications.

To significantly boost the amplifier's performance, the core design was augmented with two key features. A cascode circuit (utilizing transistors M6 and M5) was implemented to dramatically increase the output resistance and, consequently, the open-loop DC voltage gain. Following this, AC analysis was performed to evaluate the frequency response. To ensure closed-loop stability and control the Unity Gain Bandwidth (GBW), a load capacitor (CL) was added to create a dominant pole, achieving the necessary Phase Margin (PM) for a stable, high-gain amplifier.

Phase 1: DC Analysis

Circuit Schematic:

 

Circuit Details:

- All the MOSFETS are 180nm (check the library)
- M1, M2 (input NMOS diff pair): $W=20\mu$ $L=1\mu$ — decent g_m , moderate current.
- M3 (PMOS diode reference): $W=40\mu$ $L=1\mu$ — larger so the mirror can source required current.
- M4 (PMOS mirror to output): $W=40\mu$ $L=1\mu$ — match M3 W/L .
- M5 (NMOS tail current source): $W=10\mu$ $L=2\mu$ — longer L to increase output resistance and make it more current-source-like.
- $VDD = 1.8V$
- VIN common-mode ($VINP$ & $VINN$) = $0.9V$ ($VDD/2$)
- $VBIAS$ (M5 gate): $0.8V$; (sweep $0.2V \rightarrow 1.6V$ in steps to find a tail current that biases MOSFETs properly.)

Output:

```
ngspice 1 -> print i(m1) i(m2) i(m3) i(m4) i(m5)
Error: no such function as i

ngspice 2 -> print @m1[id] @m2[id] @m3[id] @m4[id] @m5[id]
@m1[id] = 7.722613e-06
@m2[id] = 7.722613e-06
@m3[id] = 7.722613e-06
@m4[id] = 7.722613e-06
@m5[id] = 1.544523e-05
ngspice 3 -> print v(out) v(vinp) v(vinn) v(vbias) v(vdd)
v(out) = 8.534765e-01
v(vinp) = 9.000000e-01
v(vinn) = 9.000000e-01
v(vbias) = 8.000000e-01
v(vdd) = 1.800000e+00
ngspice 4 ->
```


Transistor	Drain Current (Id)	Notes
M1	7.72 μ A	Input differential pair transistor
M2	7.72 μ A	Input differential pair transistor
M3	7.72 μ A	Load transistor (PMOS active load)
M4	7.72 μ A	Load transistor (PMOS active load)
M5	15.44 μ A	Tail current source (twice each side — matches sum of M1 and M2 currents)

Node	Voltage
VOUT	0.853 V
VINP	0.9 V
VINN	0.9 V
VBIAS	0.8 V
VDD	1.8 V

The output suggests that DC biasing is correct. All transistors are in saturation region as all are conducting. M5 tail current is fine. **in the linear region**, not stuck at rail, so all transistors are conducting. No MOSFET is off or in cutoff.

Phase 2: AC analysis


Circuit Schematic:

 


Circuit Details: (Additional details)

- M6 (cascode NMOS): W=10u L=2u (Same as from the 180nm library).
- VDD: DC source 1.8 V.
- VINP: Two voltage sources connected (in series) to VINP — DC = 0.9 V, AC = 1 (AC amplitude 1 V, phase = 0).
- VINN: Two voltage sources connected (in series) to VINN — DC = 0.9 V, AC = 1 (AC amplitude 1 V, phase = 180).
- VBIAS : DC source to set M5 gate (if using active tail) — 0.8 V.
- VBCAS : DC source for cascode gate (M6) — start 1.0 V
- I1 (ideal): Current source — DC = 15.44e-6 (15.44 μ A).

Output:

 

 Above fig shows frequency response. The marked plot shows the -3dB roll-off point/ pole.



Above plot is the output plot, since $V_{in} = 1V$, the plot for gain vs frequency is same.

Conclusion

The designed **5-Transistor CMOS OTA** was successfully implemented and simulated using eSim. The **DC operating point analysis** confirmed that all transistors were properly biased in their active regions, ensuring correct circuit operation. The **AC analysis** demonstrated the expected amplifier behavior — with increasing gain at low frequencies and a stable region at higher frequencies — confirming that the OTA functions effectively as a **differential voltage-to-current amplifier**. Overall, the project achieved its objective of designing and verifying the performance of a compact CMOS OTA using open-source VLSI design tools.

GitHub Repository link:

https://github.com/neeraj17-p/OTA_IITB_esim_Marathon

GitHub Readme link https://github.com/neeraj17-p/OTA_IITB_esim_Marathon/blob/main/README.md